
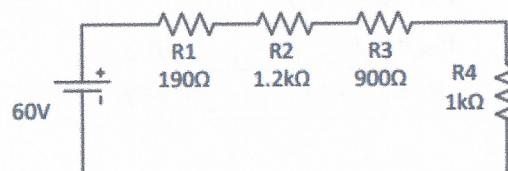


Intro to Digital Fabrication

Electronics Problem Set 1

1

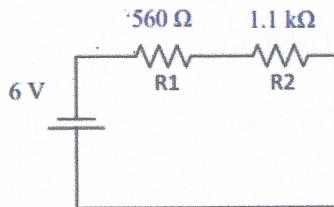Use the following circuits to practice analyzing series resistance. Determine the requested information and sketch the minimized equivalent circuit



$$R_T = 560\Omega + 1.1\text{ k}\Omega = 1.66\text{ k}\Omega$$

$$I_T = 6V / 1.66\text{ k}\Omega = 0.0036\text{ A}$$

$$V_{R1} = 0.0036\text{ A} \times 560\Omega = 2.024\text{ V}$$

$$V_{R2} = 0.0036\text{ A} \times 1100\Omega = 3.975\text{ V}$$

$$P_{R1} = 2.024\text{ V} \times 0.0036\text{ A} = 0.007\text{ W}$$

$$P_{R2} = 3.975\text{ V} \times 0.0036\text{ A} = 0.014\text{ W}$$

$$P_T = 6V \times 0.0036\text{ A} = 0.021\text{ W}$$

$$R_T = 190 + 1200 + 900 + 1000 = 3.29\text{ k}\Omega$$

$$I_T = 60V / 3.29\text{ k}\Omega = 0.018\text{ A}$$

$$V_{R1} = 0.018 \times 190\Omega = 3.4\text{ V}$$


$$V_{R2} = 0.018 \times 1200\Omega = 21.8\text{ V}$$

$$V_{R3} = 0.018 \times 900\Omega = 16.4\text{ V}$$


$$V_{R4} = 0.018 \times 1000\Omega = 18.0\text{ V}$$

$$P_T = 60V \times 0.018\text{ A} = 1.094\text{ W}$$

Sketch the equivalent circuit:

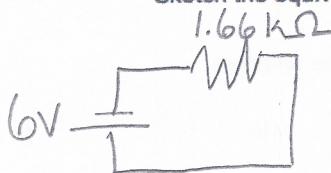

Sketch the equivalent circuit:

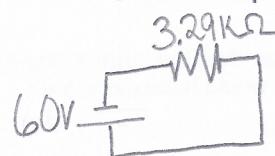

2

Use the following circuits to practice analyzing parallel resistance. Determine the requested information and sketch the minimized circuits.

$$R_T = 9.705 \Omega$$

$$I_T = 5V / 9.705 \Omega = 0.5151 A$$


$$I_{R1} = 5V / 10\Omega = .5 A$$

$$I_{R2} = 5V / 330\Omega = 0.01515 A$$

$$P_{R1} = 5V \times .5A = 2.5W$$

$$P_{R2} = 5V \times 0.01515 A = 0.075W$$

$$P_T = 5V \times 0.5151 A = 2.5757W$$

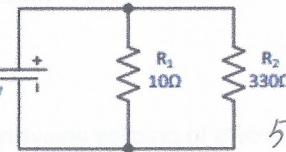

$$5V \parallel 9.705 \Omega$$

$$\frac{1}{R_T} = \frac{1}{10\Omega} + \frac{1}{330\Omega} = 0.10303$$

$$R_T = 58.44 \Omega$$


$$I_T = 36V / 58.44 \Omega = 0.616A$$

$$I_{R1} = 36V / 90\Omega = 0.4A$$

$$I_{R2} = 36V / 200\Omega = 0.18A$$

$$I_{R3} = 36V / 1000\Omega = 0.036A$$

$$P_T = 36V \times 0.616A = 22.176W$$

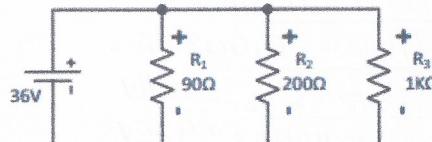

$$\frac{1}{R_T} = \frac{1}{90} + \frac{1}{200} + \frac{1}{1000} = 0.01711$$

$$R_T = \frac{1}{0.01711} = 58.44 \Omega$$

Is the total resistance larger than the largest single resistor or smaller than the smallest resistor? Is this what you would have expected?

Smaller than the smallest resistor. Yes, this is what I expected because I watched your video

Does the total current equal the sum of the currents through each resistor?

Yes, as with the second example above;  $I_T = I_1 + I_2 + I_3$

$$= 0.616A = 0.4A + 0.18A + 0.036A$$


3

Analyze the circuits to determine the following. Sketch the minimized equivalent circuit.


$$R_T = 94.285 \Omega$$

$$I_T = 0.106 A$$

$$P_T = 1.06 W$$

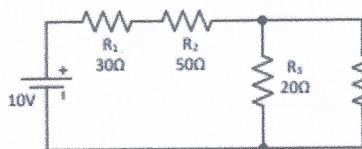

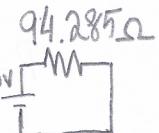
$$R_T = 10 \parallel \frac{30+50}{2} = 14.285 \Omega$$



$$R_T = 87.61 \Omega$$

$$I_T = 0.137 A$$


$$P_T = 1.643 W$$

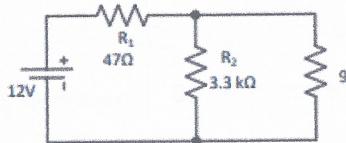

$$R_T = 12 \parallel 87.61 \Omega$$

4

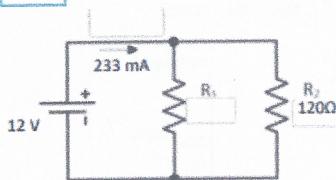Determine the value for the missing component in the following circuits.




$$A_2 = \frac{12V}{120\Omega} = 0.1A$$

$$A_T - A_2 = A_1 = 0.133 A$$

$$A_1 = \frac{12V}{X\Omega} = 0.133 A$$

$$X = \frac{12}{0.133} = 90.23 \Omega$$

$$R_1 = 90.23 \Omega$$

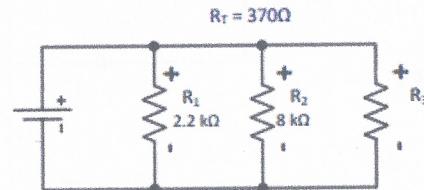

$$R_T = 370 \Omega$$


$$\frac{1}{R_T} = \frac{1}{370} = 0.0027$$

$$0.0027 - \frac{1}{2200} - \frac{1}{8000} = 0.000998$$

$$R_3 = \frac{1001.84 \Omega}{0.000998} = 1001.84 \Omega$$


5 Calculate the equivalent resistance of the following compound circuit
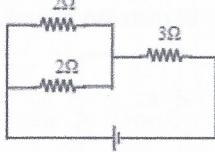
$$R_T = \frac{1}{\frac{1}{2} + \frac{1}{2}} + 3 = 4\Omega$$



6 Calculate the equivalent resistance R and the total current I.
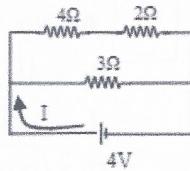
$$R_T = \frac{1}{\frac{1}{4} + \frac{1}{3}} = 2.18\Omega$$




$$I_T = \frac{4}{2.18} = 1.83A$$

7 Calculate the equivalent resistance R and the total current I

$$R_T = \frac{1}{\frac{1}{2} + \frac{1}{4}} + 1 = 2.33\Omega$$


$$I_T = \frac{4}{2.33} = 3A$$

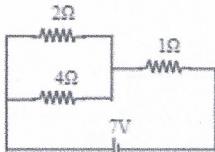

9 Calculate the equivalent resistance R and the total current I

$$R_T = \frac{1}{\frac{1}{10} + \frac{1}{20}} + 15 = 30\Omega$$

$$I_T = \frac{12V}{30\Omega} = 0.4A$$

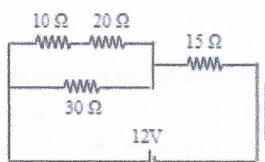


8 Calculate the the total current I, total voltage V and V<sub>2</sub>. R<sub>T</sub> = 2Ω

$$\frac{V_T}{R_1} = I_1 = 4 = \frac{X}{3} \Rightarrow X = 12V$$

$$I_T = \frac{12V}{2\Omega} = 6, I_2 = I_T - I_1$$

$$= 6 - 4 = 2A$$

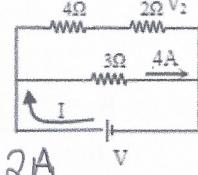


$$V = 2V$$

10 Calculate the R<sub>2</sub>, and I<sub>2</sub>

$$I_2 = 0.66A$$

$$R_2 = 30$$

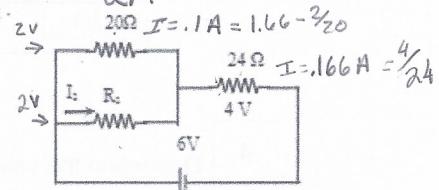

$$I = .1A = 1.66 - \frac{2}{20}$$


$$I = .166A = \frac{4}{24}$$

11 Calculate the I<sub>2</sub>, R<sub>3</sub>, the total current I.

$$I_2 = \frac{3V}{3\Omega} = 1A$$

$$R_3 = 6\Omega$$


$$I_T = 1.5A$$

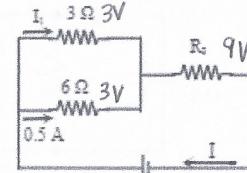

12 Calculate the the total current I and total voltage V.

$$I_T = 0.2A$$


$$V = 3 + 3 = 6V$$

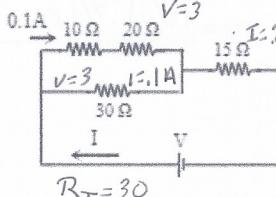

13 Calculate the the total current I and total voltage V.

$$I_T = 0.4A$$

$$V = 12V$$

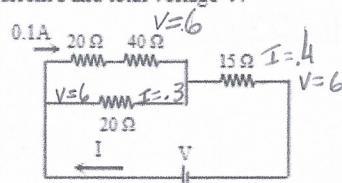

14 If R<sub>1</sub> = R<sub>2</sub>, calculate the R<sub>1</sub>, I<sub>1</sub>, and the total current I.


$$R_1 = 10\Omega$$

$$I_1 = 0.05A$$

$$R_T = 12\Omega$$

$$I_2 = 0.05A$$

$$I_T = 0.1A$$

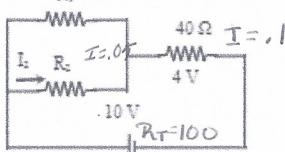


15 Use the diagram to calculate a) the total resistance in the circuit, b) the total current through the circuit, c) the total power the circuit consume, and d) the current through R<sub>2</sub>. (where R<sub>1</sub> = 10Ω, R<sub>2</sub> = 30Ω, R<sub>3</sub> = 30Ω, R<sub>4</sub> = 15Ω, V = 12V)

$$R_T = 40\Omega$$

$$I_T = 0.3A$$

$$P_T = 3.6W$$

$$I_2 = 0.15A$$

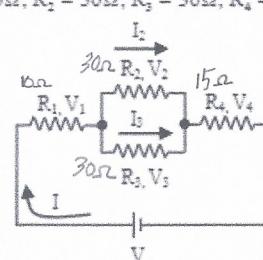

16

Find the equivalent resistance for the following set of connected resistors:

